АиЛОВТ Д/З

Полховский Артём. Гр 950503

Задание 1.

F 1	F2	F3	F 4	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

$$\mathbf{k0} = \begin{pmatrix} 0001 \\ 0010 \\ 0111 \\ 1000 \\ 1010 \\ 1101 \\ 1111 \end{pmatrix} \qquad \mathbf{k1} = \begin{pmatrix} -010 \\ -111 \\ 11-1 \end{pmatrix}$$

Задание 2.

1) 3И

x1	x2	х3	f
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$\mathbf{K}_0 = \begin{bmatrix} 111 \end{bmatrix}$$

2) 3И-НЕ

x1	x2	x3	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$k0 = \begin{pmatrix} 000 \\ 001 \\ 010 \\ 011 \\ 100 \\ 101 \\ 110 \end{pmatrix} \qquad k1 = \begin{pmatrix} 00-\\ 0-0 \\ -00 \\ 0-1 \\ -01 \\ 01-\\ -10 \end{pmatrix} \qquad k2 = \begin{pmatrix} 0--\\ -0-\\ -0-\\ 0-1 \\ 0-1 \end{pmatrix}$$

3) ИЛИ-НЕ:

x1	x2	x3	f
0	0	0	1
0	0	1	0
0	1	0	0

0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$$\mathbf{K0} = \boxed{000}$$

4) 2XOR:

x1	x2	f
0	0	1
0	1	0
1	0	0
1	1	1

$$\mathbf{K0} = \begin{bmatrix} 00 \\ 11 \end{bmatrix}$$

Задание 3.

